

# Direct Current Electricity

14-1

## Equivalent Units

$$\begin{array}{l} A = W/V = N/T \cdot m \\ C = J/V = N \cdot m/V \\ F = C/V = C^2/J = C^2/N \cdot M \\ H = V \cdot s/A = T \cdot m^2/A \\ J = N \cdot m = V \cdot C = C^2/F \\ N = J/m = V \cdot C/m \\ T = N \cdot s/C \cdot m = N/A \cdot m \\ V = W/A = C/F = J/C \\ W = J/s = V \cdot A = V^2/\Omega \\ Wb = V \cdot s = H \cdot A = T \cdot m^2 \end{array}$$

# Direct Current Electricity

---

14-2

## Basic Complex Algebra

Review FERM Ch. 43 and Mathematics Lesson 1.

## Electrostatics

### Charges

1 Coulomb (C) = charge on  $6.24 \times 10^{18}$  electrons

Charge on 1  $e^-$  =  $1.6022 \times 10^{-19}$  C (the inverse of 1 Coulomb)

### Force on Charged Object

- General case:  $\mathbf{F} = Q\mathbf{E}$  43.17
- Specific for 2 point charges:  $\mathbf{F}_2 = Q_2\mathbf{E}_1 = \frac{Q_1Q_2}{4\pi\epsilon r^2} \mathbf{a}$  43.18
  - $\mathbf{a}$  is a unit vector pointing from point charge 1 to point charge 2.

## Electrostatics

### Permittivity

$$\epsilon_r = \frac{\epsilon}{\epsilon_0} = \frac{\phi_{\text{actual}}}{\phi_{\text{vacuum}}}$$

$$\epsilon = \epsilon_r \epsilon_0$$

NOTE: On the FE exam, assume the permittivity is  $\epsilon_0 = 8.85 \times 10^{-12}$  F/m unless another value is provided.

## Electrostatics

### Electric Field Intensity

- Due to a point charge  $Q_1$ :  $\mathbf{E} = \frac{Q_1}{4\pi\epsilon r^2} \mathbf{a}$  43.20
- For a line charge  $\rho_L$ :  $\mathbf{E}_L = \frac{\rho_L}{2\pi\epsilon r} \mathbf{a}$  43.21
  - $\mathbf{a}$  is a unit vector normal to the line.
- For a sheet charge  $\rho_S$ :  $\mathbf{E}_S = \frac{\rho_S}{2\epsilon} \mathbf{a}$  43.22
  - $\mathbf{a}$  is a unit vector normal to the sheet charge.

# Direct Current Electricity

14-3d

## Electrostatics

Example (FEIM):

A point charge of 0.001 C is placed 10 m from a sheet charge of  $-0.001 \text{ C/m}^2$ , and a 10 m diameter sphere of charge 0.001 C is placed half-way in between on a straight line, all in a vacuum. What is the force on the point charge?

$$\begin{aligned}\mathbf{F} &= \mathbf{F}_{\text{sheet}} + \mathbf{F}_{\text{sphere}} = Q_{\text{point}} (\mathbf{E}_{\text{sheet}} + \mathbf{E}_{\text{sphere}}) \\ F &= Q_{\text{point}} \left( \frac{\rho_{\text{sheet}}}{2\epsilon} + \frac{Q_{\text{sphere}}}{4\pi\epsilon r^2} \right) = \left( \frac{0.001 \text{ C}}{8.85 \times 10^{-12} \frac{\text{F}}{\text{m}}} \right) \left( -\frac{0.001 \frac{\text{C}}{\text{m}^2}}{2} + \frac{0.001 \text{ C}}{4\pi(5 \text{ m})^2} \right) \\ &= -5.61 \times 10^4 \text{ N}\end{aligned}$$

## Electrostatics

Electric Flux – Gauss' Law

$$Q_{\text{encl}} = \oiint_S \epsilon \mathbf{E} \cdot d\mathbf{S} \quad 43.24$$

If  $\mathbf{E}$  is constant and parallel to  $d\mathbf{S}$ , then

$$Q_{\text{encl}} = \int_S \epsilon \mathbf{E} \cdot d\mathbf{S} = \epsilon E \int d\mathbf{S}$$

## Electrostatics

Work ( $W$ ) done by moving a charge  $Q_1$  radially from distance  $r_1$  to  $r_2$  in an electric field:

$$W = -Q_1 \int_{r_1}^{r_2} \mathbf{E} \cdot d\mathbf{L} \quad 43.25$$

- For a uniform field, the work done by moving a charge  $Q$  a distance  $d$  parallel to the uniform field:

$$\begin{aligned} W &= -\mathbf{F} \cdot \mathbf{d} = -EQd \\ &= \frac{-V_{\text{plates}} Qd}{r} \\ &= -Q\Delta V \quad 43.27 \end{aligned}$$

Note that Eq. 43.27 is always true, for all fields. ( $V$  may not be easy to compute.)

## Electrostatics

### Voltage

- A scalar quantity that describes the electrical field.
- The field  $\mathbf{E}$  is the gradient of the voltage,  $V$ .
- The voltage differential between two points is the work to bring a unit charge from one point to the other.
- The choice of zero potential is arbitrary.
- Electric field strength between two parallel plates:

$$E = \frac{V}{d} \quad 43.28$$

## Electrostatics

Example (FEIM):

A source at zero potential emits electrons at negligible velocity. An open grid at 18 V is located 0.003 m from the source. At what velocity will the electrons pass through the grid?

- (A) 490 m/s
- (B) 16 000 m/s
- (C)  $8.3 \times 10^5$  m/s
- (D)  $2.5 \times 10^6$  m/s

# Direct Current Electricity

14-3g2

## Electrostatics

The mass of an electron is  $9.11 \times 10^{-31}$  kg.

The work done by the grid on an electron is equal to the change in kinetic energy of the electron and is equal to the charge on the electron times the change in voltage potential.

$$W = \frac{1}{2}mv^2 = q\Delta V$$

$$v = \sqrt{\frac{2q\Delta V}{m}} = \sqrt{\frac{(2)(1.6022 \times 10^{-19} \text{ C})(18 \text{ V})}{9.11 \times 10^{-31} \text{ kg}}}$$
$$= 2.516 \times 10^6 \text{ m/s} \quad (2.5 \times 10^6 \text{ m/s})$$

Therefore, the answer is (D).

## Current

Change in charge per unit time

$$i(t) = \frac{dq(t)}{dt} \quad 43.29$$

Current Density ( $\rho$ )

- The density of charge moving per unit time through a volume

Volume Current Density (**J**)

- The vector current density

## Magnetism

Magnetic field around a current-carrying wire

$$\mathbf{H} = \frac{\mathbf{B}}{\mu} = \frac{I}{2\pi r} \mathbf{a} \quad \text{[straight wire]} \quad 43.35$$

Force on current-carrying conductor

$$\mathbf{F} = I\mathbf{L} \times \mathbf{B} \quad 43.36$$

# Direct Current Electricity


14-5b

## Magnetism

Example (FEIM):

A magnetic field of 0.0005 T makes a 30° angle with a 1 m wire carrying 0.05 A. What is the force on the wire?

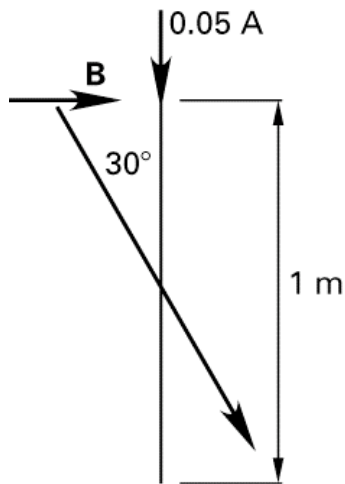- (A)  $1.25 \times 10^{-5}$  N
- (B)  $5.00 \times 10^{-4}$  N
- (C)  $1.25 \times 10^{-3}$  N
- (D)  $2.50 \times 10^{-3}$  N



$$\begin{aligned} |\mathbf{F}| &= I|\mathbf{L} \times \mathbf{B}| = I|\mathbf{L}||\mathbf{B}|\sin\theta \\ &= (0.05 \text{ A})(1 \text{ m})(0.0005 \text{ T})(\sin 30^\circ) \\ &= 1.25 \times 10^{-5} \text{ N} \end{aligned}$$

Therefore, the answer is (A).

## Induced Voltage

Also called *electromotive force* (emf)

For  $N$  loops:

$$v = \frac{-N d\phi}{dt} = -NBL \frac{ds}{dt} \quad 43.41$$

# Direct Current Electricity

14-7a

## DC Circuits

Resistivity

$$R = \frac{\rho L}{A} \quad 44.1$$

Depends on temperature:

$$R = R_0(1 + \alpha(T - T_0)) \quad 44.3$$

$$\rho = \rho_0(1 + \alpha(T - T_0)) \quad 44.2$$

Example (FEIM):

A cube with an edge length of 0.01 m has resistivity of 0.01  $\Omega \cdot \text{m}$ .

What is the resistance from one side to the opposite side?

- (A) 0.0001
- (B) 0.001
- (C) 0.1
- (D) 1

$$R = \frac{\rho L}{A} = \frac{(0.01 \Omega \cdot \text{m})(0.01 \text{m})}{(0.01 \text{m})^2} = 1 \Omega$$

Therefore, the answer is (D).

# Direct Current Electricity

14-7b

## DC Circuits

Ohm's Law

$$V = IR \quad 44.22$$

Resistors in Series:  $R_{\text{eq}} = R_1 + R_2 + \cdots + R_n \quad 44.4$

Resistors in Parallel:  $R_{\text{eq}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}} \quad 44.5$

Equivalent resistance of two resistors in parallel:

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \quad 44.6$$

Resistive Power  $P = VI = \frac{V^2}{R} = I^2 R \quad 44.7$


# Direct Current Electricity

14-7c

## DC Circuits

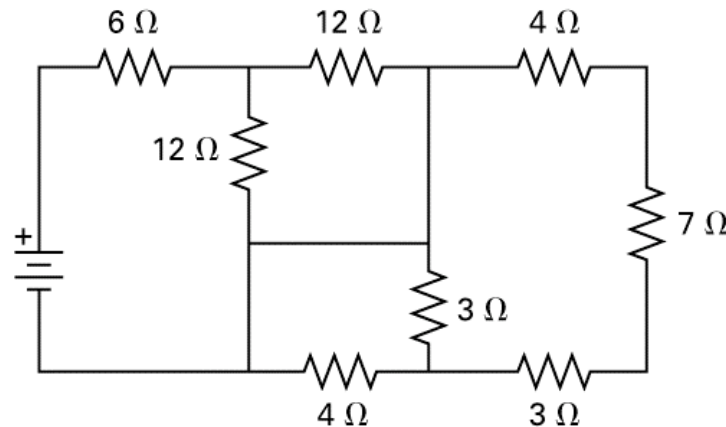Example (FEIM):

What is the resistance of the following circuit as seen from the battery?



No current will flow through the two  $4\ \Omega$  resistors, the two  $3\ \Omega$  resistors, or the  $7\ \Omega$  resistor. The circuit reduces to one  $6\ \Omega$  in series with two  $12\ \Omega$  in parallel.

$$R = 6\ \Omega + 6\ \Omega = 12\ \Omega$$

## DC Circuits

### Kirchhoff's Laws

- Voltage Law (KVL)

$$\sum V_{\text{rises}} = \sum V_{\text{drops}} \quad 44.24$$

- Current Law (KCL)

$$\sum I_{\text{in}} = \sum I_{\text{out}} \quad 44.23$$

## DC Circuits

### Loop Current Circuit Analysis

1. Select one less than the total number of loops.
2. Write Kirchhoff's voltage equation for each loop.
3. Use the simultaneous equations to solve for the current you want.


# Direct Current Electricity

14-7f

## DC Circuits

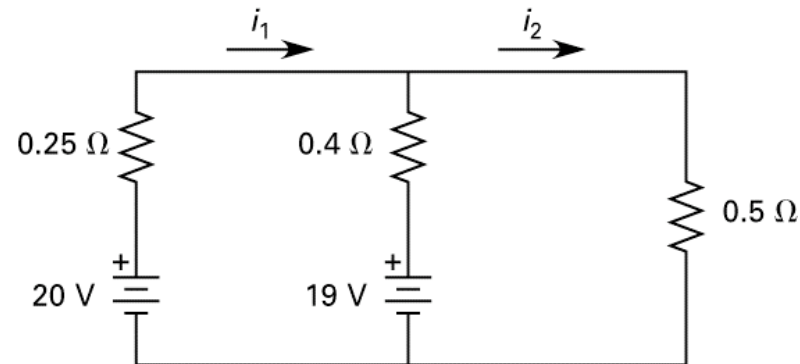Example (FEIM):

Find the current through the  $0.5 \Omega$  resistor.



The voltage sources around the left loop are equal to the voltage drops across the resistances.

$$20 \text{ V} - 19 \text{ V} = 0.25 \Omega i_1 + 0.4 \Omega (i_1 - i_2)$$

The same is true for the right loop.

$$19 \text{ V} = 0.4 \Omega (i_2 - i_1) + 0.5 \Omega i_2$$

Solve—two equations and two unknowns.

$$0.65 \Omega i_1 - 0.4 \Omega i_2 = 1 \text{ V}$$

$$-0.4 \Omega i_1 + 0.9 \Omega i_2 = 19 \text{ V}$$

$$i_1 = 20 \text{ A}$$

$$i_2 = 30 \text{ A}$$

The current through the  $0.5 \Omega$  resistor is 30 A.

## DC Circuits

### Node Voltage Circuit Analysis

1. Convert all current sources to voltage sources.
2. Choose one node as reference (usually ground).
3. Identify unknown voltages at other nodes compared to reference.
4. Write Kirchhoff's current equation for all unknown nodes except reference node.
5. Write all currents in terms of voltage drops.
6. Write all voltage drops in terms of the node voltages.


# Direct Current Electricity

14-7h

## DC Circuits

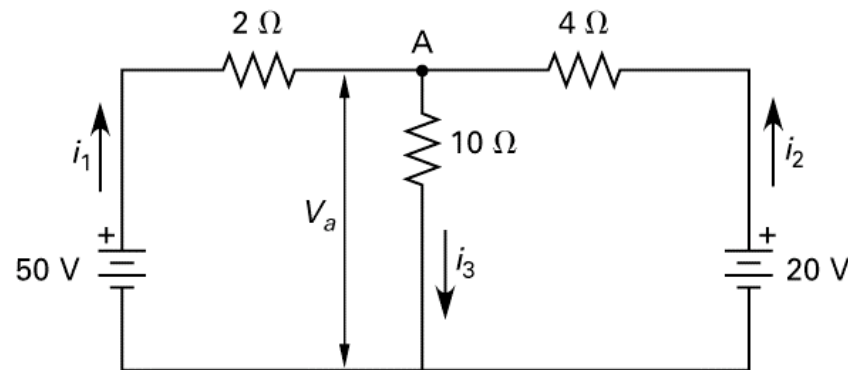Example (FEIM):

Find the voltage potential at point A and the current  $i_1$ .



$$i_1 + i_2 = i_3$$

$$\frac{50 \text{ V} - V_A}{2 \Omega} + \frac{20 \text{ V} - V_A}{4 \Omega} = \frac{V_A - 0}{10 \Omega}$$

$$V_A = 35.3 \text{ V}$$

$$i_1 = \frac{50 \text{ V} - V_A}{2 \Omega} = \frac{50 \text{ V} - 35.3 \text{ V}}{2 \Omega} \\ = 7.35 \text{ A}$$

## Voltage Divider

The voltage across a resistor  $R$  in a loop with total resistance  $R_{\text{total}}$  with a voltage source  $V$  is

$$V_R = \frac{R}{R_{\text{total}}} V$$

In the general case, the voltage on impedance  $Z_i$  in a loop with total impedance  $Z_{\text{total}}$  with a voltage source  $v$  is

$$V_i = \frac{Z_i}{Z_{\text{total}}} v$$

NOTE: Each symbol is a complex number in the general case.


# Direct Current Electricity

14-8b

## Voltage Divider

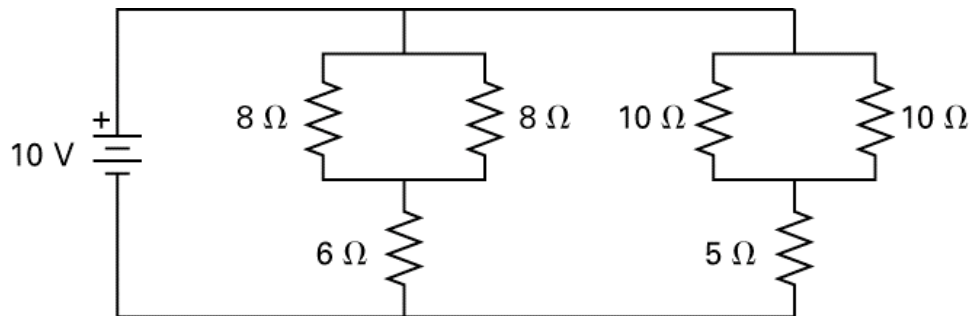Example (FEIM):

What is the voltage across the  $6\ \Omega$  resistor?



- (A) 5 V
- (B) 6 V
- (C) 8 V
- (D) 10 V

Two  $8\ \Omega$  resistors in parallel equal  $4\ \Omega$ .

The voltage across the  $6\ \Omega$  resistor is

$$(10\ \text{V}) \left( \frac{6\ \Omega}{6\ \Omega + 4\ \Omega} \right) = 6\ \text{V}$$

Therefore, the answer is (B).

## Current Divider

The current through a resistor  $R$  in parallel with another resistance  $R_{\text{parallel}}$  and a current into the node of  $I$  is:

$$I_R = \frac{R_{\text{parallel}}}{R_{\text{total}}} I \quad (\text{Resistance } R \text{ does not appear explicitly. } R_{\text{total}} \text{ is the sum of the resistances in parallel.})$$

In the general case, the current through impedance  $Z_i$  connected to a node in parallel with total impedance  $Z_{\text{total}}$  with a current  $i$  into the node is:

$$i_{Z_i} = \frac{Z_{\text{parallel}}}{Z_{\text{total}}} i \quad (Z_{\text{total}} \text{ is the sum of the impedances in parallel.})$$

NOTE: Each symbol is a complex number in the general case.

Procedure:

1. Identify the component you want the current through.
2. Simplify the circuit.
3. Determine the current into the node that is connected to the component of interest.
4. Allocate current in proportion to the reciprocal of resistance.

# Direct Current Electricity

14-9b


## Current Divider

Example (FEIM):

What is the current through the  $6\ \Omega$  resistor?

- (A)  $1/10\ \text{A}$
- (B)  $1/3\ \text{A}$
- (C)  $1/2\ \text{A}$
- (D)  $1\ \text{A}$

$$i = i_1 + i_2$$

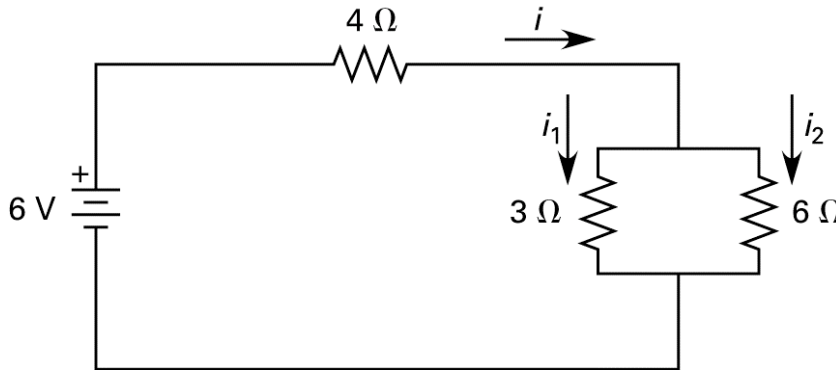

Simplify the circuit.

$3\ \Omega$  in parallel with  $6\ \Omega = 2\ \Omega$

$2\ \Omega$  in series with  $4\ \Omega = 6\ \Omega$

$$i = \frac{6\ \text{V}}{6\ \Omega} = 1\ \text{A}$$

$$R_{\text{parallel}} = 3\ \Omega$$

$$R_{\text{total}} = 3\ \Omega + 6\ \Omega = 9\ \Omega$$

$$i = (1\ \text{A}) \left( \frac{3\ \Omega}{3\ \Omega + 6\ \Omega} \right) = 1/3\ \text{A}$$

Therefore, the answer is (B).

## Superposition Theorem

The net current/voltage is the sum of the current/voltage caused by each current/voltage source.

Procedure:

1. Short all voltage sources, and open all current sources, then turn on only one source at a time.
2. Simplify the circuit to get the current/voltage of interest.
3. Repeat until all sources have been used.
4. Add the results for the answer.


# Direct Current Electricity

14-10b

## Superposition Theorem

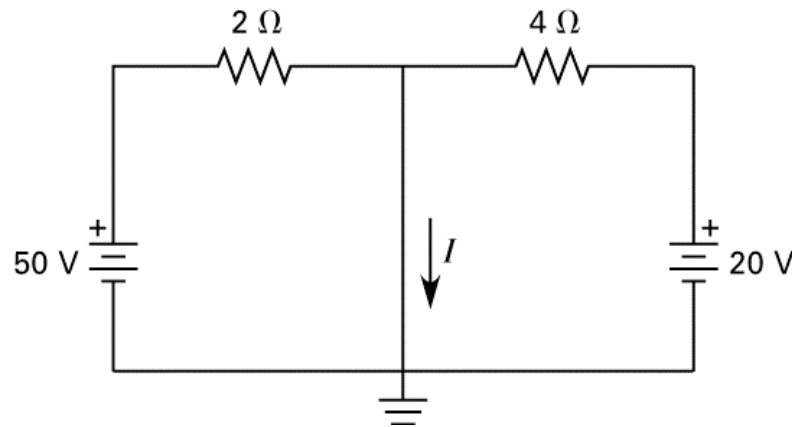Example (FEIM):

Determine the current through the center leg of the circuit.



$$\text{Short the 20 V source. } I = 50 \frac{\text{V}}{2 \Omega} = 25 \text{ A}$$

$$\text{Short the 50 V source. } I = 20 \frac{\text{V}}{4 \Omega} = 5 \text{ A}$$


$$I_{\text{total}} = 25 \text{ A} + 5 \text{ A} = 30 \text{ A}$$

# Direct Current Electricity


14-11a

## Norton Equivalent


Figure 44.4 Norton Equivalent Circuit

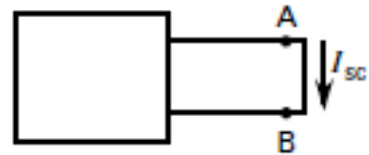

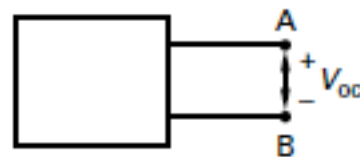step 1: Measure short-circuit current between terminals A and B.



step 2: Measure open-circuit voltage.

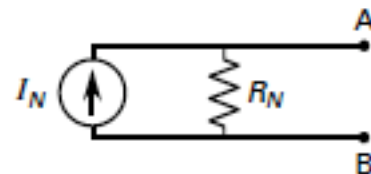

step 3: Draw the Norton equivalent.

$$R_N = R_{eq}$$

$$I_N = I_{sc}$$

$$V_{oc} = V_A - V_B \quad 44.36$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} \quad 44.37$$


# Direct Current Electricity

14-11b

## Norton Equivalent

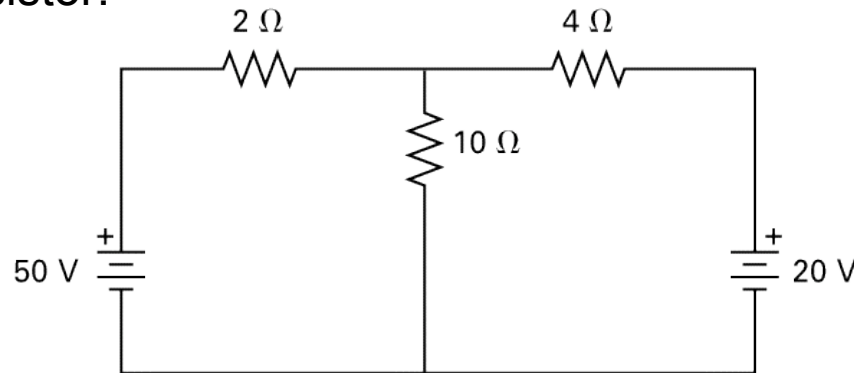Example (FEIM):

Find the Norton equivalent current and resistance of the circuit as seen by the  $10\ \Omega$  resistor.



With the  $10\ \Omega$  resistor open circuited, and the voltage sources shorted, the circuit is  $4.0\ \Omega$  and  $2.0\ \Omega$  in parallel.

$$R_N = (2\ \Omega) \left( \frac{4\ \Omega}{2\ \Omega + 4\ \Omega} \right) = 1.33\ \Omega$$

With the  $10\ \Omega$  resistor shorted, the circuit looks just like the previous example.


$$I_N = 30\ \text{A}$$

# Direct Current Electricity

# 14-12a


## Thevenin Equivalent

Figure 44.3 Thevenin Equivalent Circuit

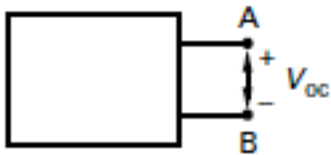


step 1: Measure open-circuit voltage.

$$V_{oc} = V_A - V_B \quad 44.36$$

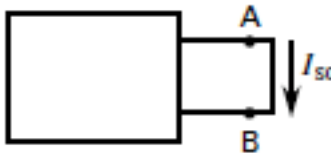

step 2: Measure short-circuit current between terminals A and B.

$$R_N = R_{Th} \quad 44.38$$

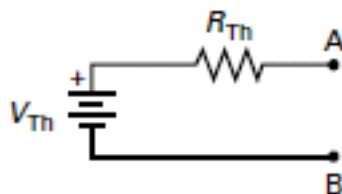

step 3: Draw the Thevenin equivalent.

$$V_{Th} = I_N R_N \quad 44.39$$

$$I_N = \frac{V_{Th}}{R_{Th}} \quad 44.40$$

$$R_{Th} = R_{eq}$$
$$V_{Th} = V_{oc}$$


# Direct Current Electricity

14-12b1

## Thevenin Equivalent

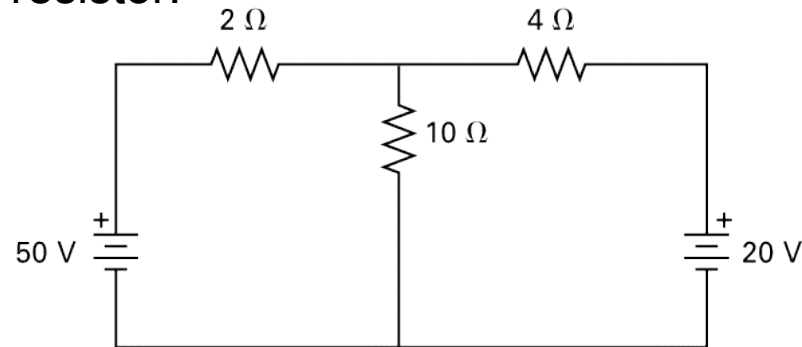Example (FEIM):

Find the Thevenin equivalent voltage and resistance of the circuit as seen by the  $10\ \Omega$  resistor.




The Thevenin resistance is the same as the Norton resistance in the previous example, which is  $1.3\ \Omega$ . With the  $10\ \Omega$  resistor open-circuited, apply the Kirchhoff voltage law around the loop and find  $V_{TH} = 40\ \text{V}$ .

# Direct Current Electricity

14-12b2

## Thevenin Equivalent

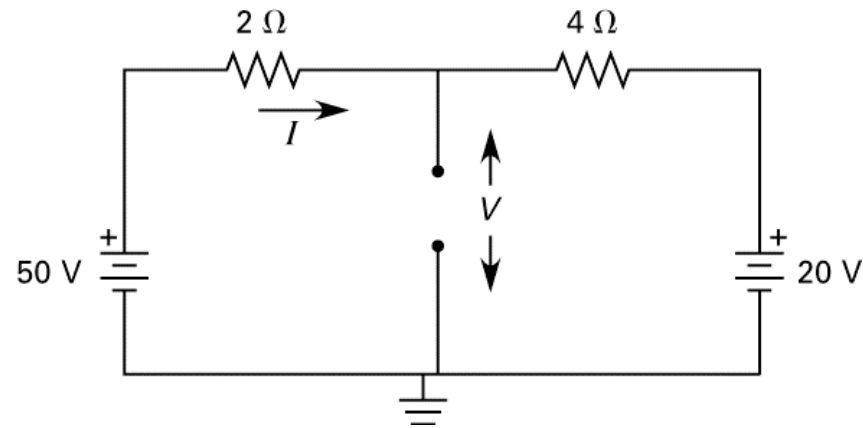

$$(50 \text{ V} - 20 \text{ V}) = I(2 \Omega + 4 \Omega)$$

$$I = 5 \text{ A}$$

$$\begin{aligned} V &= 50 \text{ V} - I(2 \Omega) \\ &= 50 \text{ V} - (5 \text{ A})(2 \Omega) \\ &= 40 \text{ V} \end{aligned}$$

## Capacitors

$$q_C(t) = Cv_C(t) \quad [\text{varying } v(t)] \quad 44.9$$

$$\begin{aligned} \text{energy} &= \frac{CV^2}{2} = \frac{VQ}{2} \\ &= \frac{Q^2}{2C} \end{aligned} \quad 44.13$$

### Parallel Plate Capacitors

$$C = \frac{\epsilon A}{d} \quad 44.10$$

- Capacitance in Parallel:

$$C_{\text{eq}} = C_1 + C_2 + \cdots + C_n \quad 44.19$$

- Capacitance in Series:

$$C_{\text{eq}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}} \quad 44.18$$


# Direct Current Electricity

14-13b

## Capacitors

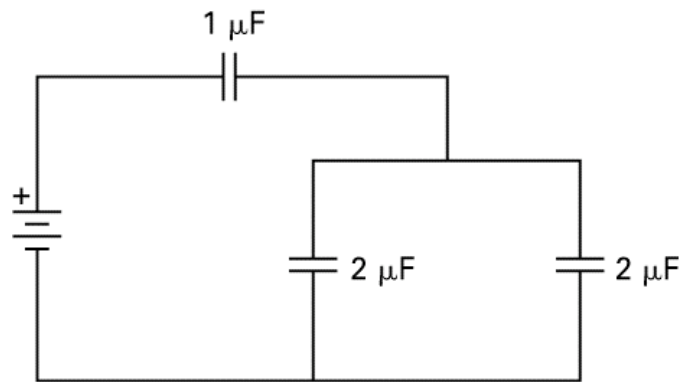Example 1 (FEIM):

What is the capacitance seen by the battery?



The two  $2 \mu\text{F}$  capacitors in parallel are equivalent to  $4 \mu\text{F}$ . The  $1 \mu\text{F}$  capacitor in series with the equivalent  $4 \mu\text{F}$  capacitance will add as resistors in parallel.

$$\begin{aligned} C &= \frac{C_1 C_2}{C_1 + C_2} \\ &= \frac{(1 \mu\text{F})(4 \mu\text{F})}{1 \mu\text{F} + 4 \mu\text{F}} \\ &= \frac{4}{5} \mu\text{F} \end{aligned}$$

## Capacitors

Example 2 (FEIM):

A 10  $\mu\text{F}$  capacitor has been connected to a potential source of 150 V. The energy stored in the capacitor in 10 time constants is most nearly

- (A)  $1.0 \times 10^{-7}$  J
- (B)  $9.0 \times 10^{-3}$  J
- (C)  $1.1 \times 10^{-1}$  J
- (D)  $9.0 \times 10^1$  J

$$\begin{aligned}\text{Energy} &= \frac{(10 \times 10^{-6} \text{ F})(150 \text{ V})^2}{2} \\ &= 0.11 \text{ J} \quad (1.1 \times 10^{-1} \text{ J})\end{aligned}$$

Therefore, the answer is (C).

## Inductors

$$v_L(t) = L \frac{dI(t)}{dt} \quad 44.15$$

$$L = \frac{N\phi}{I} \quad 44.14$$

$$i_L = i_L(0) + \frac{1}{L} \int_0^t v_L(\tau) d\tau \quad 44.16$$

- Inductance in Series:

$$L_{\text{eq}} = L_1 + L_2 + \cdots + L_n \quad 44.20$$

- Inductance in Parallel:

$$L_{\text{eq}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_n}} \quad 44.21$$


# Direct Current Electricity

14-14b

## Inductors

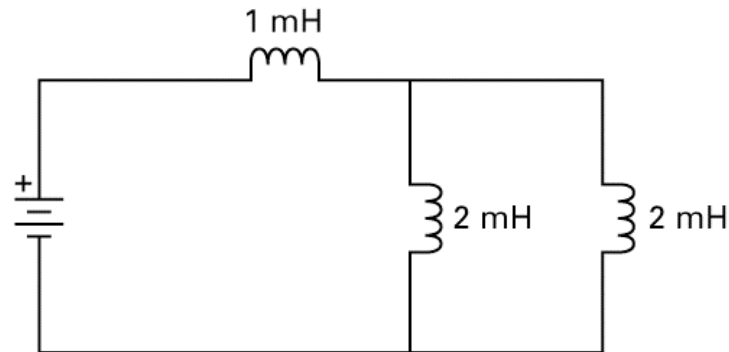Example (FEIM):

Find the inductance as seen from the battery.



The two 2 mH inductors in parallel will add as resistors in parallel.

$$L = \frac{L_1 L_2}{L_1 + L_2} = \frac{(2 \text{ mH})(2 \text{ mH})}{2 \text{ mH} + 2 \text{ mH}} = 1 \text{ mH}$$


The 1 mH inductor in series with the equivalent 1 mH inductance will combine for 2 mH total inductance.

# Direct Current Electricity

14-15a

## RC Transients


Figure 44.5 RC Transient Circuit

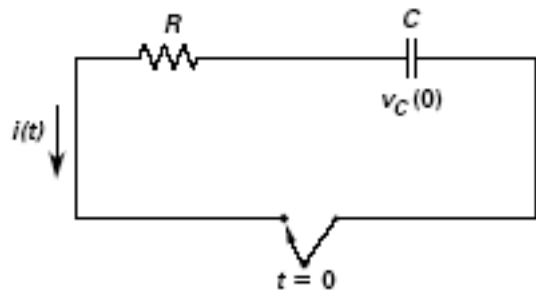

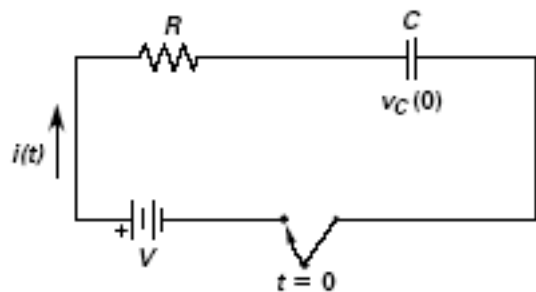(a) series-RC, discharging  
(energy source(s) disconnected)

$$v_C(t) = v_C(0)e^{-t/RC} + V \left(1 - e^{-t/RC}\right) \quad 44.45$$

$$i(t) = \left(\frac{V - v_C(0)}{R}\right) e^{-t/RC} \quad 44.46$$



(b) series-RC, charging  
(energy source(s) connected)

$$\begin{aligned} v_R(t) &= i(t)R \\ &= (V - v_C(0))e^{-t/RC} \end{aligned} \quad 44.47$$

# Direct Current Electricity


14-15b1

## RC Transients

Example (FEIM):

At  $t = 0$ , the capacitor is discharged, and the switch is moved from A to B. At  $t = 6$  s, the switch is moved to C.

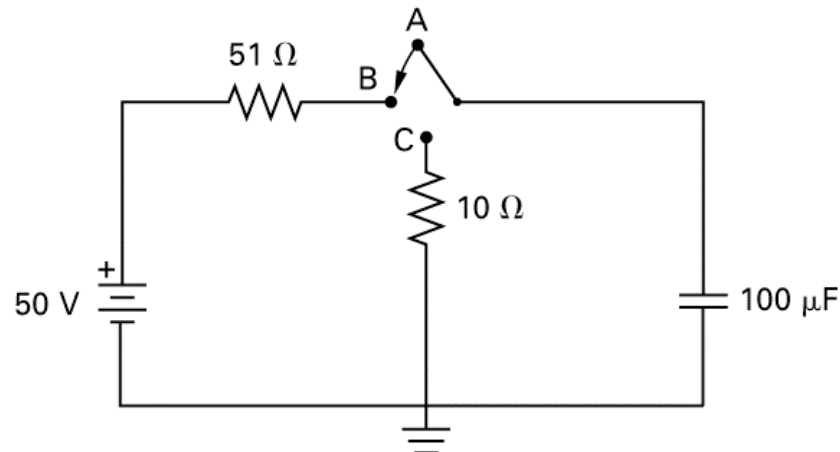- (a) What is the capacitor voltage at  $t = 6$  s?
- (b) What is the current at  $t = 10$  s?
- (c) When (after 6 s) is the voltage across the capacitor equal to 10 V?



## RC Transients

(a) From time = 0 to 6 s,

$$V_c(0) = 0$$

$$V = 50 \text{ V}$$

$$RC = (51 \times 10^3 \Omega)(100 \times 10^{-6} \text{ F}) = 5.1 \text{ s}$$

$$v_c(6 \text{ s}) = 0e^{-\frac{6 \text{ s}}{5.1 \text{ s}}} + 50 \text{ V} \left( 1 - e^{-\frac{6 \text{ s}}{5.1 \text{ s}}} \right) = 34.58 \text{ V}$$

So 34.58 V is the peak voltage the capacitor reaches before it starts to discharge.

## RC Transients

(b) From time = 6 s on,

$$V_c(6 \text{ s}) = 34.58 \text{ V}$$

$$V = 0 \text{ V}$$

$$RC = (10 \times 10^3 \Omega)(100 \times 10^{-6} \text{ F}) = 1 \text{ s}$$

$$i(10 \text{ s}) = \left( \frac{0 - 34.58 \text{ V}}{10 \times 10^3 \Omega} \right) e^{-\frac{10 \text{ s} - 6 \text{ s}}{1}} = -6.3 \times 10^{-5} \text{ A}$$

$$(c) v_c(t) = 34.58 \text{ V} e^{-\frac{t-6 \text{ s}}{1 \text{ s}}} + 0 \left( 1 - e^{-\frac{t-6 \text{ s}}{1 \text{ s}}} \right) = 10 \text{ V}$$

Take the natural logarithm of both sides of the equation

$$\ln 34.58 \text{ V} e^{-(t-6 \text{ s})} = \ln 10$$

$$\ln e^{-(t-6 \text{ s})} + \ln 34.58 \text{ V} = \ln 10$$


$$-(t - 6 \text{ s}) = \ln 10 - \ln 34.58 \text{ V}$$

$$t - 6 \text{ s} = 1.24 \text{ s}$$


$$t = 7.24 \text{ s}$$

## RL Transients

Figure 44.6 RL Transient Circuit

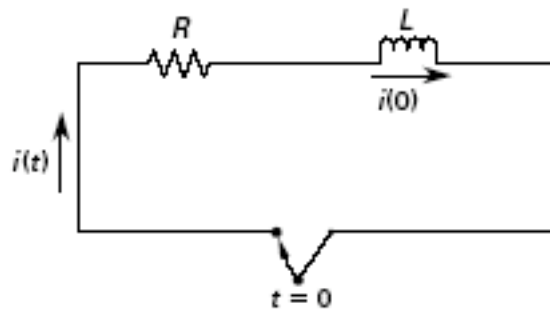

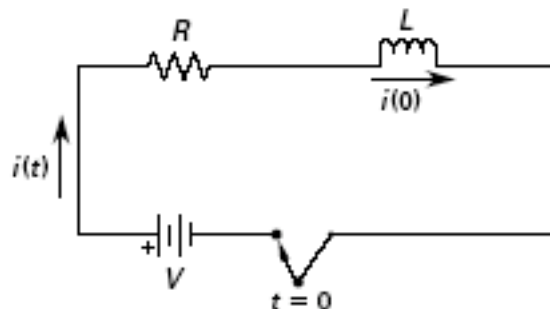(a) series-RL, discharging  
(energy source(s) disconnected)



(b) series-RL, charging  
(energy source(s) connected)

$$v_R(t) = i(t)R$$

$$= i(0)Re^{-Rt/L} + V(1 - e^{-Rt/L}) \quad 44.41$$

$$i(t) = i(0)e^{-Rt/L} + \frac{V}{R}(1 - e^{-Rt/L}) \quad 44.42$$

$$v_L(t) = L \frac{di}{dt}$$

$$= -i(0)Re^{-Rt/L} + Ve^{-Rt/L} \quad 44.43$$


# Direct Current Electricity

14-16b

## RL Transients

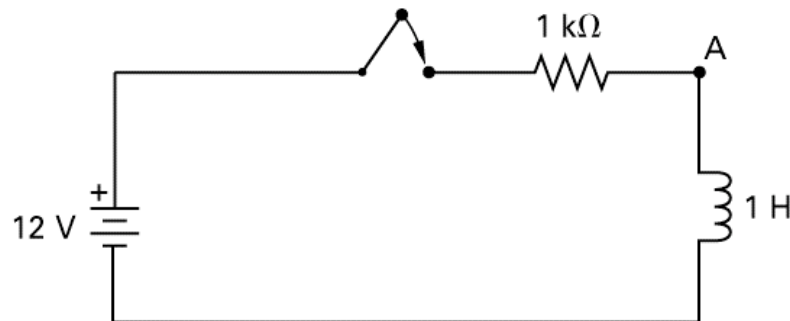Example (FEIM):

Find the voltage at point A at the instant the switch is closed. The switch has been open for a long time, and there is no initial current in the inductor.



- (A) 0 V
- (B) 1 V
- (C) 3 V
- (D) 12 V

$$i(0) = 0$$

$$V = 12\text{ V, so at } t = 0$$

$$v_L(0^+) = 0Re^0 + (12\text{ V})e^0 = 12\text{ V}$$

Therefore, the answer is (D).

## Transducers

A transducer is any device used to convert a physical phenomenon into an electrical signal (e.g., microphone, thermocouple, and voltmeter).

Characteristics of measurement design:

- Sensitivity
- Linearity
- Accuracy
- Precision
- Stability

## Resistance Temperature Detectors (RTDs)

Make use of changes in their resistance to determine the changes in temperature.

$$R_T \approx R_0 (1 + \alpha (T - T_0)) \quad 49.3$$

Example (FEIM):

A resistance temperature detector (RTD) that is not perfectly linear is used for a temperature measurement. The temperature coefficient is  $3.900 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$ , the reference temperature is  $0^\circ\text{C}$ , and the reference resistance is  $500.0 \text{ } \Omega$ . The resistance measured when the actual temperature is  $400^\circ\text{C}$  is  $1247 \text{ } \Omega$ . Determine the error in the temperature measurement.

## Resistance Temperature Detectors (RTDs)

If the RTD was perfectly linear the resistance would be given by

$$R_T = R_0(1 + \alpha(T - T_0))$$

However, the temperature that the RTD indicates is not the actual temperature of 400°C, so rearranging the RTD equation to solve for the temperature that the RTD indicates yields

$$\begin{aligned} T &= \frac{R_T - R_0 + \alpha R_0 T_0}{\alpha R_0} \\ &= \frac{1247 \, \Omega - 500.0 \, \Omega + (3.900 \times 10^{-3} \, ^\circ\text{C}^{-1})(500^\circ\text{C})(0^\circ\text{C})}{(3.900 \times 10^{-3} \, ^\circ\text{C}^{-1})(500^\circ\Omega)} \\ &= 383.1^\circ\text{C} \end{aligned}$$

The error in the measurement is:

$$\text{Error} = 383.1^\circ\text{C} - 400^\circ\text{C} = -16.9^\circ\text{C}$$

## Strain Gages

Metal or semiconductor foils that change resistance linearly with the strain.

$$GF = \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} = \frac{\Delta R}{R \epsilon} \quad 49.6$$

Example (FEIM):

A strain gage is measured to determine the gage factor. A strain gage with an initial resistance of 200.00  $\Omega$  and final resistance of 199.79  $\Omega$  when subjected to a strain that causes the gage to compress to 0.9994 cm. The initial length of the gage was 1.0000 cm. What is the gage factor?

- (A) 0.15
- (B) 0.42
- (C) 1.8
- (D) 4.0

## Strain Gages

$$\begin{aligned} GF &= \frac{\frac{\Delta R}{R}}{\frac{\Delta L}{L}} \\ &= \frac{\frac{199.79 \Omega - 200.00 \Omega}{200.00 \Omega}}{\frac{0.9994 \text{ cm} - 1.0000 \text{ cm}}{1.0000 \text{ cm}}} \\ &= 1.75 \end{aligned}$$

Therefore, the answer is (C).

# Direct Current Electricity

14-20a


## Wheatstone Bridges

Balanced:

$$\frac{R_4}{R_1} = \frac{R_3}{R_2} \quad [\text{balanced}] \quad 49.11$$

Quarter-bridge:

Figure 49.3 Wheatstone Quarter Bridge

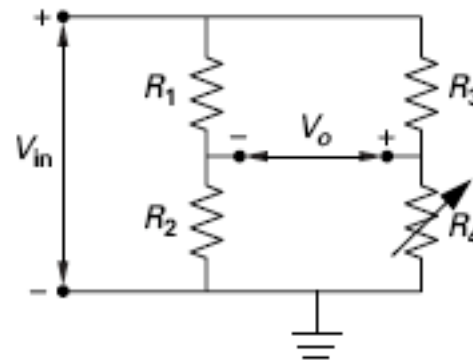

$$R_1 = R_2 = R_3 = R \quad 49.12$$

$$R_4 = R + \Delta R \quad 49.13$$

$$|\Delta R| \ll R \quad 49.14$$

$$V_o \approx \left( \frac{\Delta R}{4R} \right) V_{in} \quad 49.15$$

## Wheatstone Bridges

Example (FEIM):

There are three high-precision resistors known to be  $10.00 \text{ k}\Omega$  in a quarter bridge circuit.  $R_1$  is a sensor with a small resistance difference from  $10 \text{ k}\Omega$ . Find the resistance if  $V_{\text{in}} = 5.00 \text{ V}$  and  $V_o = 0.03 \text{ V}$ .

$$\begin{aligned}\Delta R &= \frac{4RV_o}{V_{\text{in}}} \\ &= \frac{(4)(10.00 \text{ k}\Omega)(0.03 \text{ V})}{5.00 \text{ V}} \\ &= 0.24 \text{ k}\Omega\end{aligned}$$

$$R_1 = 10.00 \text{ k}\Omega + 0.24 \text{ }\Omega = 10.24 \text{ k}\Omega$$

For the strain gage quarter-bridge circuit,  $\Delta R$  can be substituted.

$$V_o = \frac{1}{4}(\text{GF})\varepsilon V_{\text{in}}$$

# Direct Current Electricity

14-21a

## Sampling

Sampling Rate or Frequency:  $f_s = \frac{1}{\Delta t}$  49.16

### Shannon's Sampling Theorem

Determines the sampling rate to reproduce accurately in the discrete time system.

Nyquist Rate:  $f_N = 2f_I$  49.17 (where  $f_I$  is the frequency of interest)

Reproducible Sampling:

$$f_s > f_n \quad [\text{reproducible sampling}]$$

## Sampling

Example (FEIM):

An analog signal is to be sampled at  $0.03 \mu\text{s}$  intervals. What is most nearly the highest frequency that can be accurately reproduced?

- (A)  $4.0 \times 10^6 \text{ Hz}$
- (B)  $12 \times 10^6 \text{ Hz}$
- (C)  $16 \times 10^6 \text{ Hz}$
- (D)  $18 \times 10^6 \text{ Hz}$

The sampling frequency is

$$\begin{aligned} f_s &= \frac{1}{\Delta t} \\ &= \frac{1}{0.03 \times 10^{-6}} \\ &= 33 \times 10^6 \text{ Hz} \end{aligned}$$

## Sampling

The sampling frequency must be greater than the Nyquist rate for accurate reproduction.

$$f_s > 2f_N$$

The greatest frequency that can be reproduced at this sampling rate is

$$f_N < \frac{f_s}{2} = \frac{33 \times 10^6 \text{ Hz}}{2} = 16.7 \times 10^6 \text{ Hz} \quad (16 \times 10^6 \text{ Hz})$$

Therefore, the answer is (C).

## Analog-to-Digital Conversion

### Voltage Resolution

The range from a high voltage,  $V_H$ , and a low voltage,  $V_L$ , is divided up into the  $2^n$  ranges.

$$\epsilon_V = \frac{V_H - V_L}{2^n} \quad 49.19$$

For example, if all the bits are “1” then the analog value is somewhere between  $V_H$  and  $V_H - \epsilon_V$ . To calculate the analog value from the digital value use

$$V = \epsilon_V N + V_L \quad 49.20$$

## Analog-to-Digital Conversion

Example (FEIM):

A 16 bit analog-to-digital conversion has a resolution of  $1.52588 \times 10^{-4}$  V and the lowest voltage measured has half the magnitude of the highest voltage. Both the high and low voltages are positive. Determine the highest voltage.

$$\begin{aligned}V_H - V_L &= 2^n \varepsilon_v \\ &= (2)^{16} (1.52588 \times 10^{-4} \text{ V}) \\ &= 10.0 \text{ V}\end{aligned}$$

The problem statement also says that

$$|V_H| = |2V_L|$$

Since  $V_H$  and  $V_L$  are positive, this equation becomes

$$V_H = 2V_L$$

Substituting into the first equation

$$2V_L - V_L = 10 \text{ V}$$

$$V_L = 10 \text{ V}$$

$$V_H = 20 \text{ V}$$

## Measurement Uncertainty

Kline-McClintock Equation:

A method for estimating the uncertainty in a function that depends on more than one measurement.

$$w_R = \sqrt{\left(w_1 \frac{\partial f}{\partial x_1}\right)^2 + \left(w_2 \frac{\partial f}{\partial x_2}\right)^2 + \cdots + \left(w_n \frac{\partial f}{\partial x_n}\right)^2} \quad 49.21$$

## Measurement Uncertainty

Example (FEIM):

A function is given by  $R = 5x_1 - 3x_2^2$ .

Find the measurement uncertainty at (1, 2) if the uncertainty in the variables is  $\pm 0.01$  and  $\pm 0.03$  respectively.

$$\frac{\partial R}{\partial x_1} = 5 \qquad \frac{\partial R}{\partial x_2} = -6x_2$$

At the point (1, 2) the partial derivatives are

$$\left. \frac{\partial R}{\partial x_1} \right|_{(1,2)} = 5 \qquad \left. \frac{\partial R}{\partial x_2} \right|_{(1,2)} = (-6)(2) = -12$$

$$\begin{aligned} w_R &= \sqrt{\left( w_1 \left. \frac{\partial R}{\partial x_1} \right|_{(1,2)} \right)^2 + \left( w_2 \left. \frac{\partial R}{\partial x_2} \right|_{(1,2)} \right)^2} \\ &= \sqrt{\left( (0.01)(5) \right)^2 + \left( (0.03)(-12) \right)^2} \\ &= 0.36 \end{aligned}$$

## Measurement Uncertainty

If the function  $R$  is the sum of the measurements,  
 $R = x_1 + x_2 + x_3 + \dots + x_n$ , then the Kline-McClintock method reduces to

$$w_R = \sqrt{w_1^2 + w_2^2 + \dots + w_n^2}$$

This is called the *root sum square* (RSS) value.

If the function  $R$  is the sum of the measurements times constants,  
 $R = a_1x_1 + a_2x_2 + a_3x_3 + \dots + a_nx_n$ , then the Kline-McClintock method reduces to

$$w_R = \sqrt{a_1^2w_1^2 + a_2^2w_2^2 + \dots + a_n^2w_n^2}$$

This is called a *weighted RSS* value.